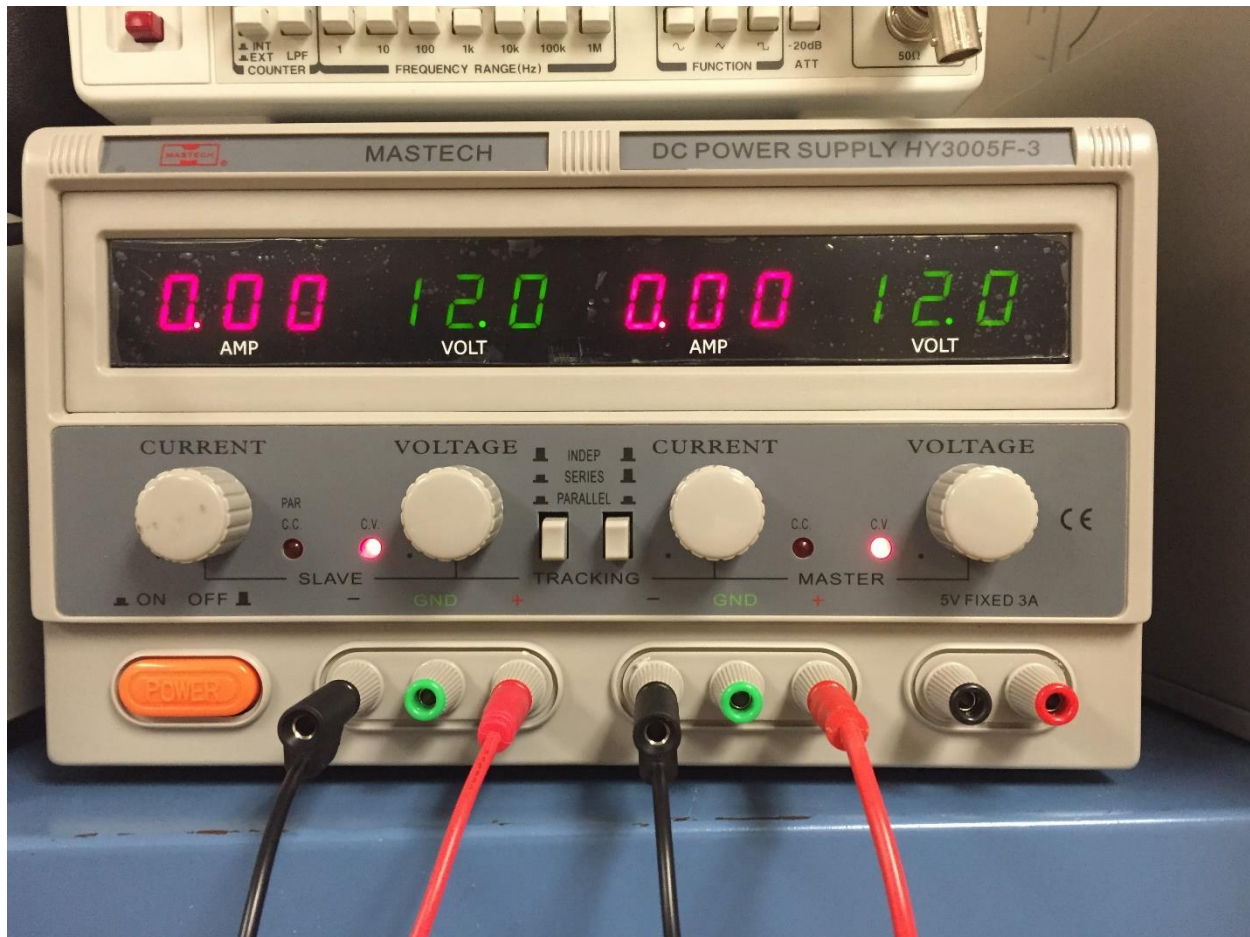


Giancarlo Paternoster
24 Volt Power Supply

It is possible to get a 24 volt potential from the bench top power supply by following these steps. Essentially, we are taking two 12 volt DC sources and wiring them together in series (much like joining two batteries end to end) in order to create an effective 24 volt source.

1. Turn on the power supply and turn both "sides" to 12 volts



2. Connect the wires as illustrated in the images

